

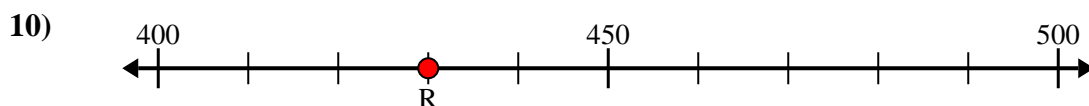
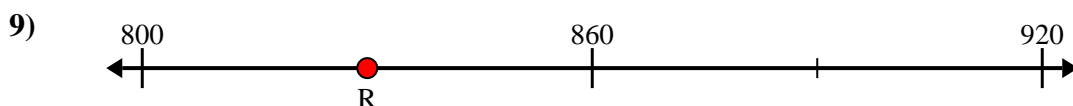
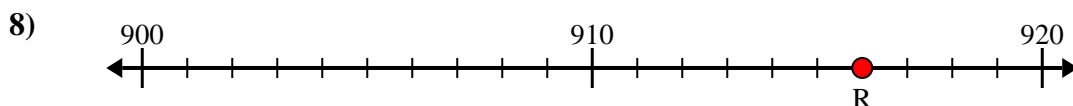
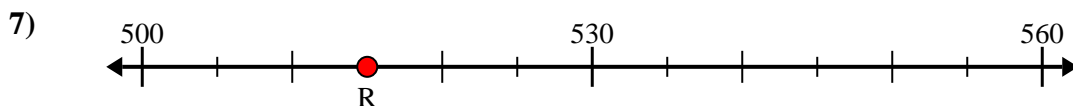
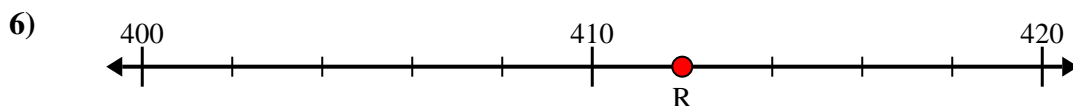
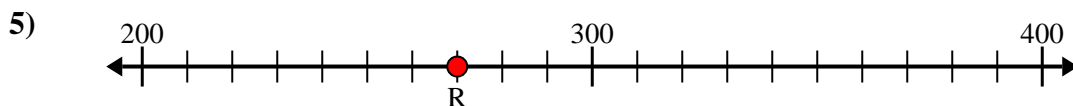
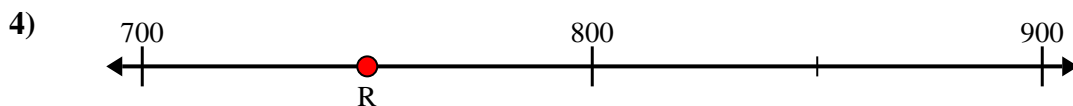
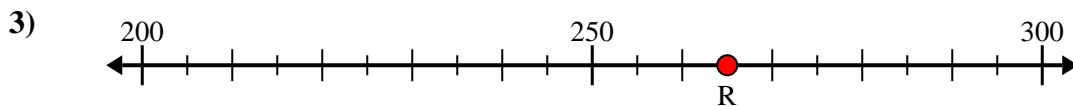


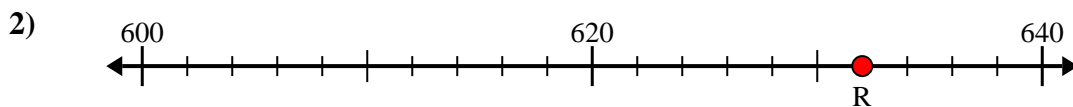

Find the value of R.










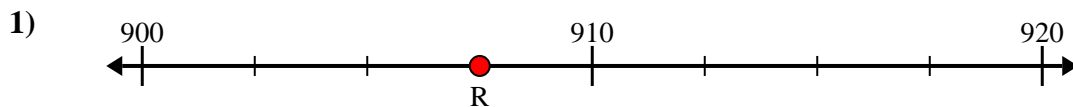


Answers

- 1. _____
- 2. _____
- 3. _____
- 4. _____
- 5. _____
- 6. _____
- 7. _____
- 8. _____
- 9. _____
- 10. _____



Find the value of R.

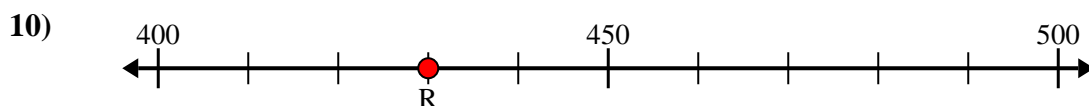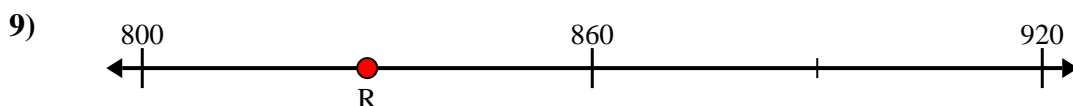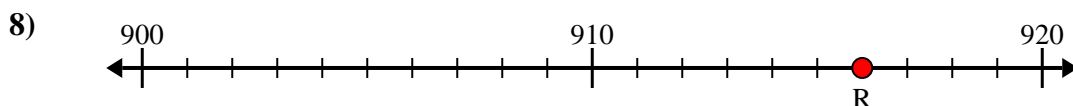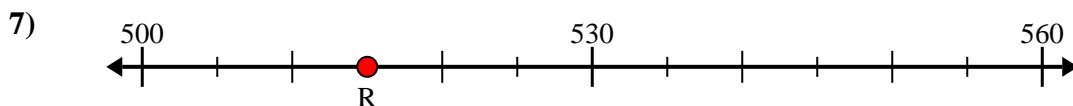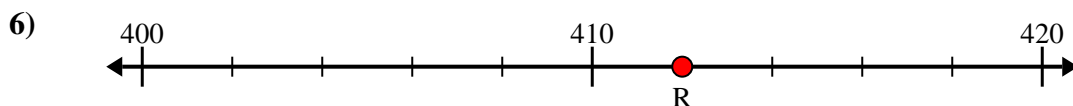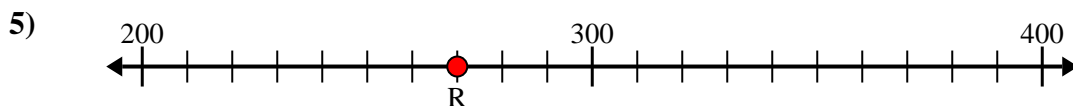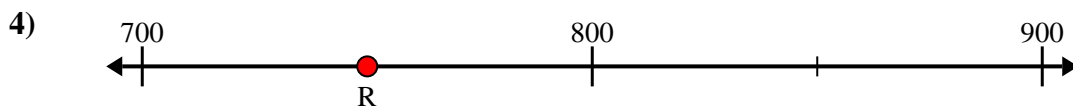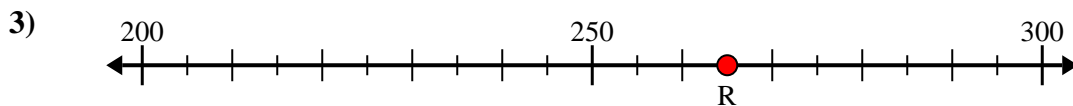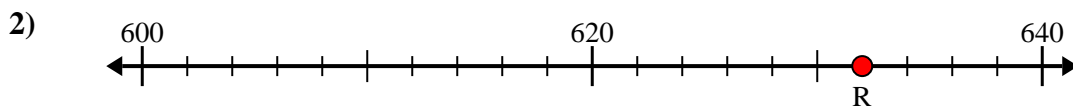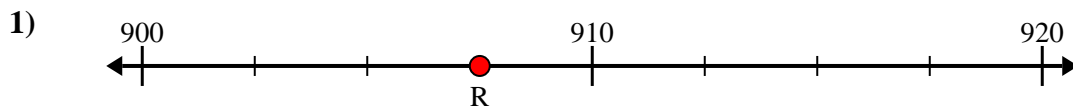

Answers

1. 907.5

2. 632

3. 265

4. 750

5. 270

6. 412

7. 515

8. 916

9. 830

10. 430