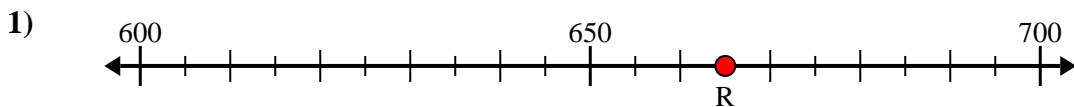





Find the value of R.


Answers




1. _____

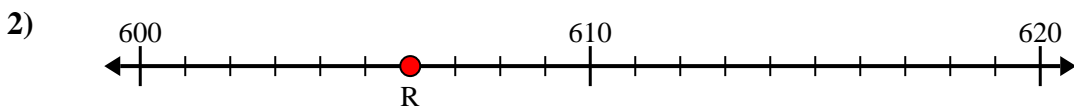


2. _____

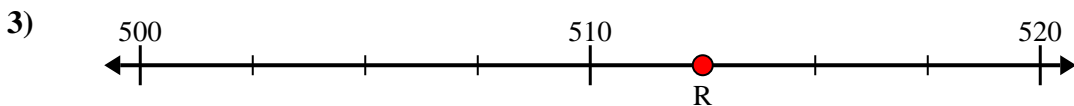


3. _____

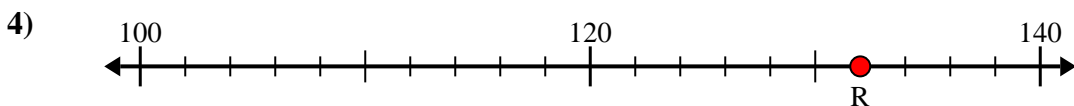


4. _____

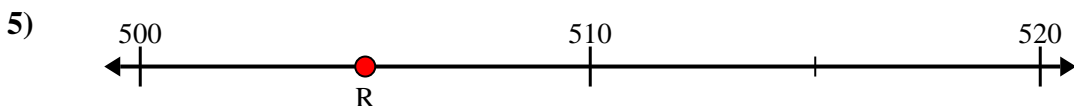


5. _____

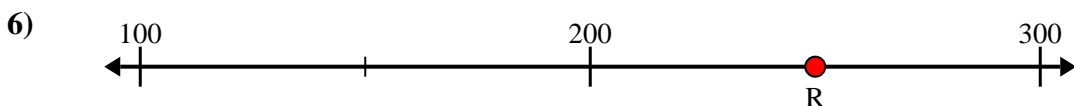


6. _____

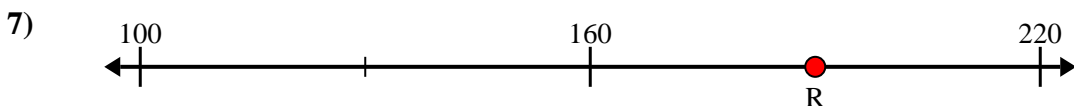


7. _____

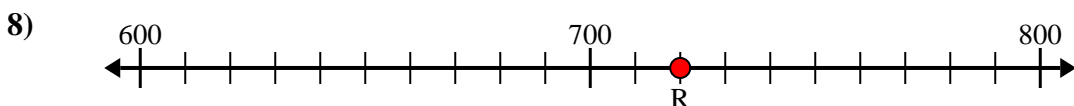

8. _____

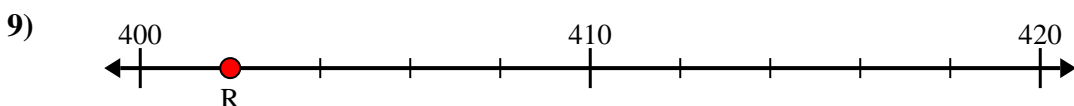











9. _____

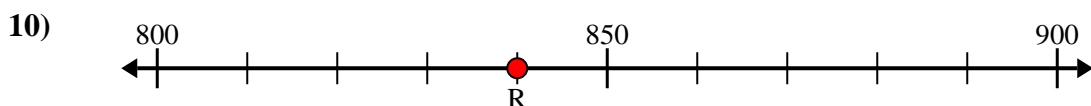

10. _____



Find the value of R.

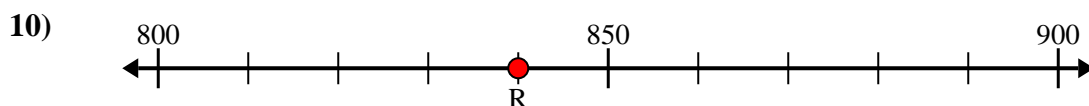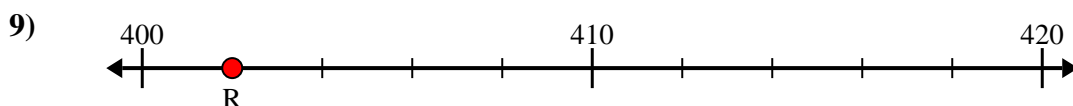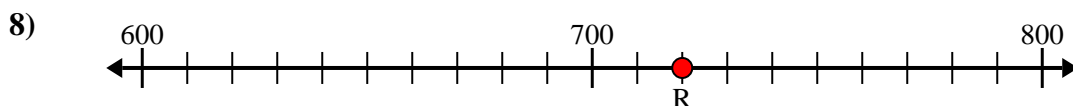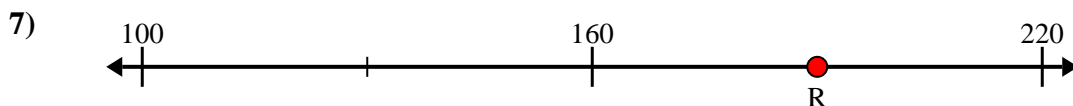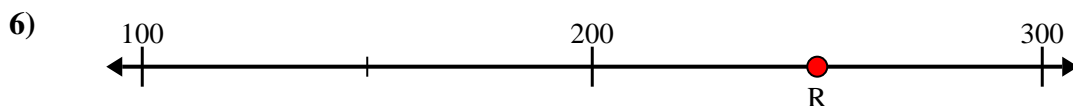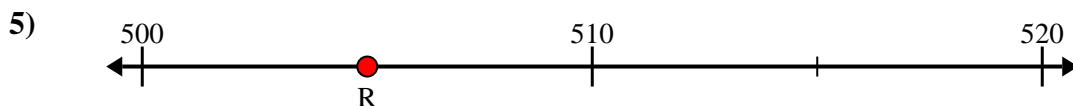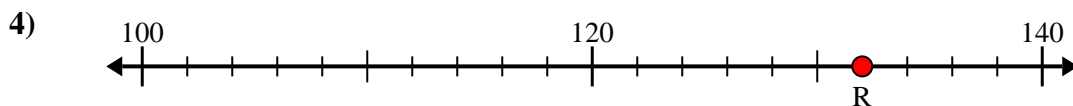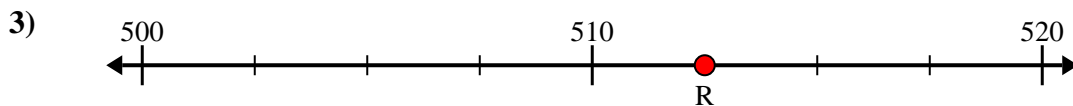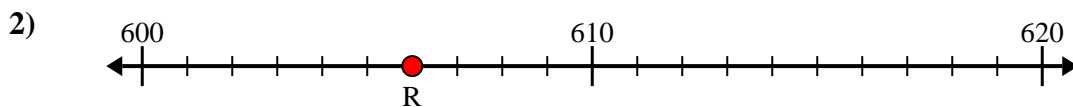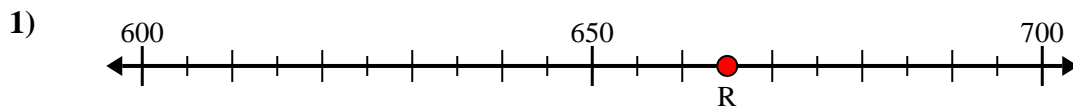

Answers

1. 665

2. 606

3. 512.5

4. 132

5. 505

6. 250

7. 190

8. 720

9. 402

10. 840