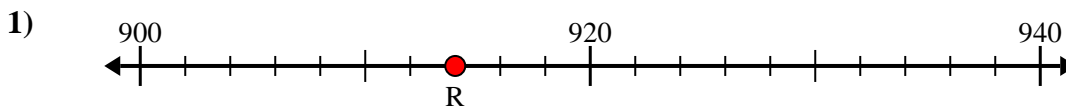





Find the value of R.


Answers




1. _____

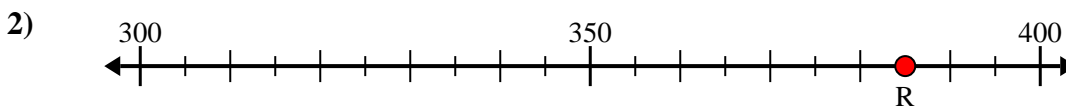


2. _____

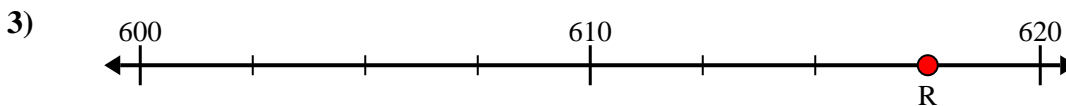


3. _____

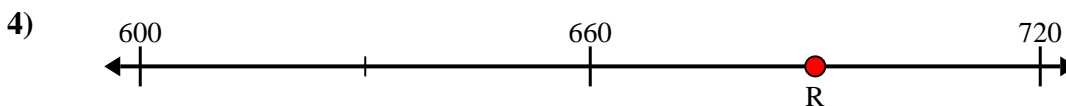


4. _____

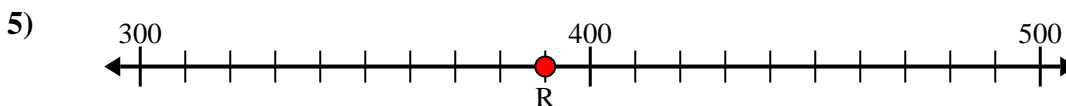


5. _____

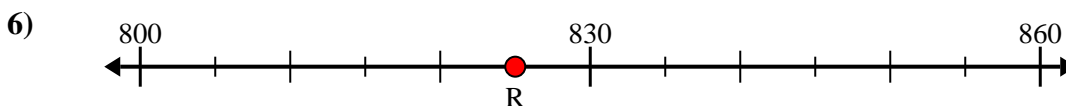


6. _____

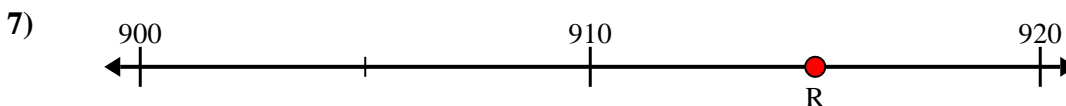


7. _____

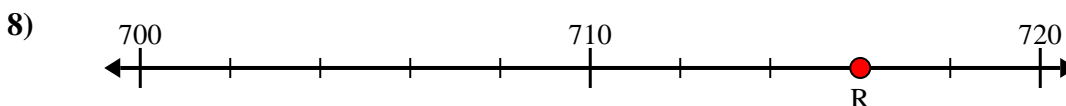

8. _____

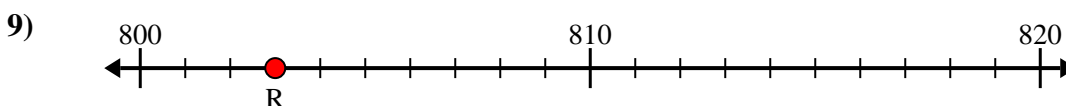











9. _____

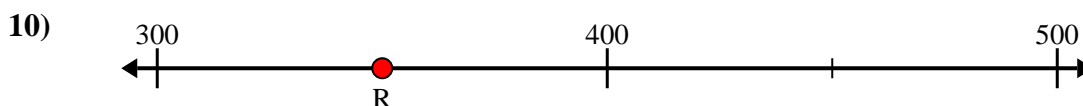

10. _____



Find the value of R.

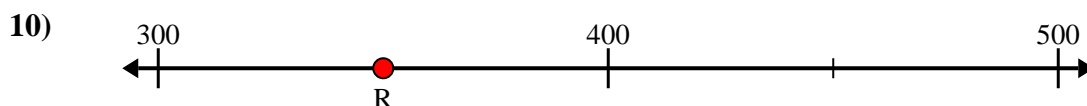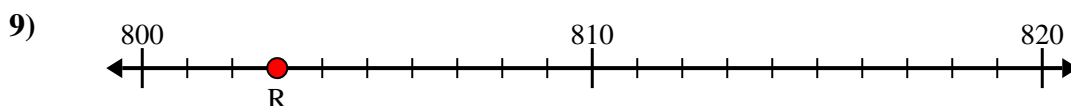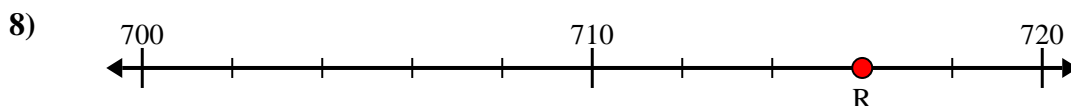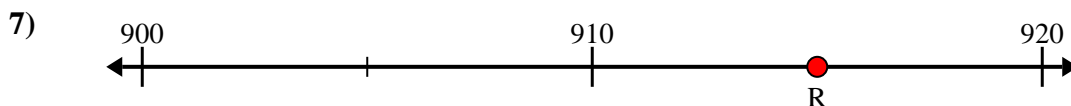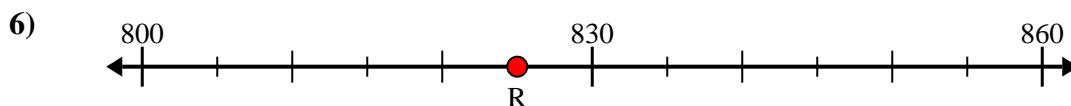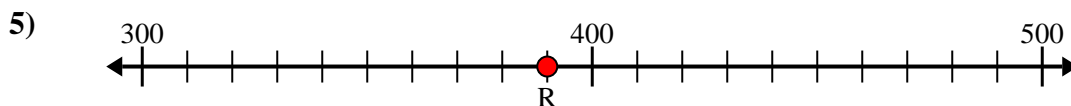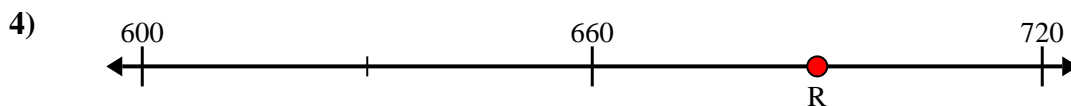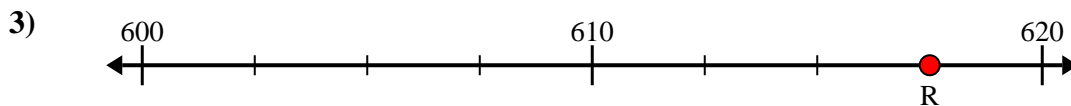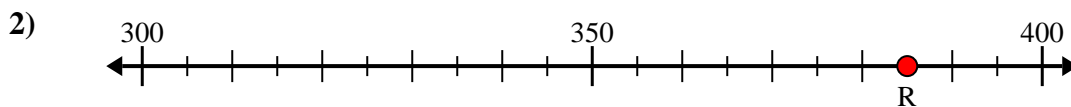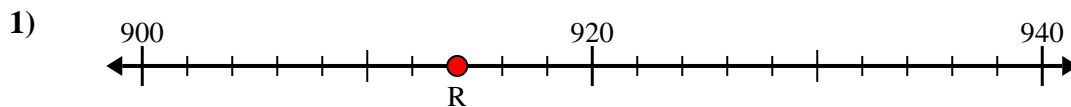Answers1. 9142. 3853. 617.54. 6905. 3906. 8257. 9158. 7169. 80310. 350